



Nemecxpetr Update README.md



1 contributor

Raw

Blame



190 lines (158 sloc) | 6.59 KB

4 Segment

Lab assignment

1. Preparation tasks (done before the lab at home). Submit:

- ☒ Figure or table with connection of 7-segment displays on Nexys A7 board,
- ☒ Decoder truth table for common anode 7-segment display.

2. Seven-segment display decoder. Submit:

- ☒ Listing of VHDL architecture from source file `hex_7seg.vhd` with syntax highlighting,
- ☒ Listing of VHDL stimulus process from testbench file `tb_hex_7seg.vhd` with syntax highlighting,
- ☒ Screenshot with simulated time waveforms; always display all inputs and outputs,
- ☐ Listing of VHDL code from source file `top.vhd` with 7-segment module instantiation.


3. LED(7:4) indicators. Submit:

- ☐ Truth table and listing of VHDL code for LEDs(7:4) with syntax highlighting,

- Screenshot with simulated time waveforms; always display all inputs and outputs.

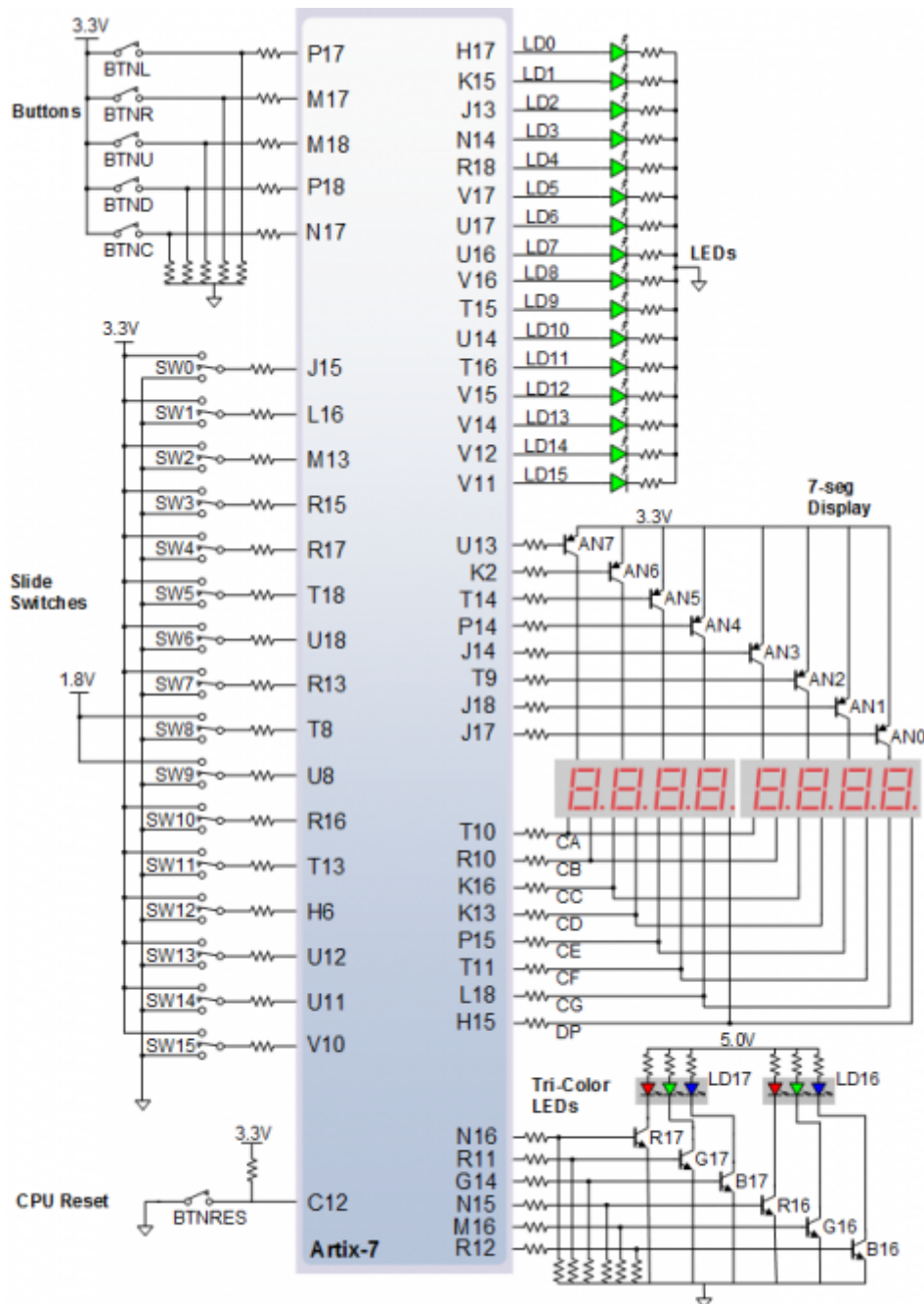1. Preparation tasks (done before the lab at home)

Schematic with connections of 7-segment display on Nexys A7-50T.



Truth table for common anode 7-segment display.

Hex	Input	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1

Hex	Input	A	B	C	D	E	F	G
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0



Figure used from [How Seven Segment Display Works & Interface it with Arduino](#).

2. Seven-segment display decoder

Listing of VHDL architecture from source file `hex_7seg.vhd`

```

-----
-- p_7seg_decoder:
-- A combinational process for 7-segment display decoder.

```

```

-- Any time "hex_i" is changed, the process is "executed".
-- Output pin seg_o(6) corresponds to segment A, seg_o(5) to B, etc.
-----
p_7seg_decoder : process(hex_i)
begin
    case hex_i is
        when "0000" =>
            seg_o <= "0000001";    -- 0
        when "0001" =>
            seg_o <= "1001111";    -- 1
        when "0010" =>
            seg_o <= "0010010";    -- 2
        when "0011" =>
            seg_o <= "0000110";    -- 3
        when "0100" =>
            seg_o <= "1001100";    -- 4
        when "0101" =>
            seg_o <= "0100100";    -- 5
        when "0110" =>
            seg_o <= "0100000";    -- 6
        when "0111" =>
            seg_o <= "0001111";    -- 7
        when "1000" =>
            seg_o <= "0000000";    -- 8
        when "1001" =>
            seg_o <= "0000100";    -- 9
        when "1010" =>
            seg_o <= "0001000";    -- A
        when "1011" =>
            seg_o <= "1100000";    -- B
        when "1100" =>
            seg_o <= "0110001";    -- C
        when "1101" =>
            seg_o <= "1000010";    -- D
        when "1110" =>
            seg_o <= "0110000";    -- E
        when others =>
            seg_o <= "0111000";    -- F
    end case;
end process p_7seg_decoder;

```

Listing of VHDL stimulus process from testbench file tb_hex_7seg.vhd

```

report "Stimulus process started" severity note;

s_hex <= "0000"; wait for 100ns;
s_hex <= "0001"; wait for 100ns;
s_hex <= "0010"; wait for 100ns;
s_hex <= "0011"; wait for 100ns;
s_hex <= "0100"; wait for 100ns;
s_hex <= "0101"; wait for 100ns;


```

```

s_hex <= "0110"; wait for 100ns;
s_hex <= "0111"; wait for 100ns;
s_hex <= "1000"; wait for 100ns;
s_hex <= "1001"; wait for 100ns;
s_hex <= "1010"; wait for 100ns;
s_hex <= "1011"; wait for 100ns;
s_hex <= "1100"; wait for 100ns;
s_hex <= "1101"; wait for 100ns;
s_hex <= "1110"; wait for 100ns;
s_hex <= "1111"; wait for 100ns;
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Screenshot with simulated time waveforms

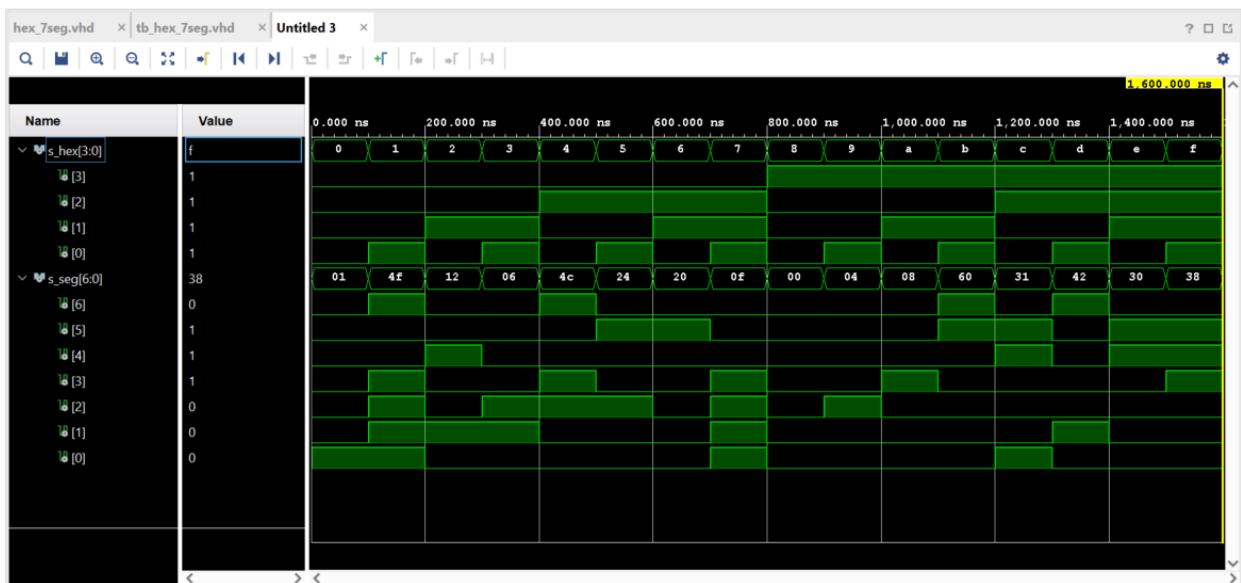

Listing of VHDL code from source file `top.vhd` with 7-segment module instantiation

```

hex2seg : entity work.hex_7seg
port map
(
    hex_i    => SW,

    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
);

```

3. LED(7:4) indicators

Truth table and listing of VHDL code for LEDs(7:4)

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0
1	0001	0	0	1	1
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
b	1011	0	1	1	0
C	1100	0	1	0	0
d	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

```
-- Display input value
```

```
LED(3 downto 0) <= SW;
```

```
-- Turn LED(4) on if input value is equal to 0, ie "0000"
```

```
LED(4) <= '1' when (SW = "0000") else '0';
```

```
-- Turn LED(5) on if input value is greater than "1001"
```

```
LED(5) <= '1' when (SW > "1001") else '0';
```

```
-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ..
```

```
LED(6) <= '1' when (SW = "0001" or SW = "0011" or SW = "0101" or SW = "0111"
```

```
-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
```

```
LED(7) <= '1' when (SW = "0001" or SW = "0010" or SW = "0100" or SW = "1000"
```

Screenshot with simulated time waveforms

