

01 - Logic gates

Lab assignment

- [x] 1. Submit the GitHub link to your Digital-electronics-1 repository.
- [x] 2. Verification of De Morgan's laws of function $f(c,b,a)$. Submit:
 - Listing of VHDL code design.vhd,
 - Screenshot with simulated time waveforms,
 - Link to your public EDA Playground example.
- [x] 3. Verification of Distributive laws. Submit:
 - Listing of VHDL code design.vhd,
 - Screenshot with simulated time waveforms,
 - Link to your public EDA Playground example.

- [] Prepare all tasks in your README file Digital-electronics-1/Labs/01-gates/README.md, export/print it to PDF, use BUT e-learning web page and submit a single PDF file. The deadline for submitting the task is the day before the next laboratory exercise.

1 Submitting GitHub repository

My GitHub [repository \(https://github.com/Nemecxpetr/Digital-electronics-1\)](https://github.com/Nemecxpetr/Digital-electronics-1).

2 Verification of De Morgan's laws of function $f(c,b,a)$

Parts:

- Listing of VHDL code design.vhd,
- Screenshot with simulated time waveforms,
- Link to your public EDA Playground example.

Function is defined as follows. We also derived the only NAND and NOR form of function via De Morgan's laws.

$$f(c,b,a) = \bar{b}a + \bar{c}\bar{b}$$

$$f(c,b,a)_{\text{NAND}} = \overline{\overline{\bar{b}a + \bar{c}\bar{b}}}$$

$$f(c,b,a)_{\text{NOR}} = \overline{\bar{b} + \bar{a} + \bar{c} + \bar{b}} = \overline{\bar{b} + \bar{a} + \bar{c} + \bar{b}}$$

Equations were generated by [Online LaTeX Equation Editor \(https://www.codecogs.com/latex/eqneditor.php\)](https://www.codecogs.com/latex/eqneditor.php).

Code from [EDU Playground \(https://www.edaplayground.com/x/DcV5\)](https://www.edaplayground.com/x/DcV5):

Excerpt from design.vhd:


```
architecture dataflow of gates is
begin
    f_o <= (not b_i and a_i) or (not b_i and not c_i);
    fnand_o <= not(not((not b_i) and a_i) and not(not c_i and not b_i));
    fnor_o <= not(b_i or not a_i) or not(c_i or b_i);
end architecture dataflow;
```

Here are the simulation results in table:

c	b	a	$f(c,b,a)$	$f(c,b,a)_{\text{nand}}$	$f(c,b,a)_{\text{nor}}$
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	0	0	0

0 1 1	0	0	0
1 0 0	1	1	1
1 0 1	1	1	1
1 1 0	0	0	0
1 1 1	0	0	0

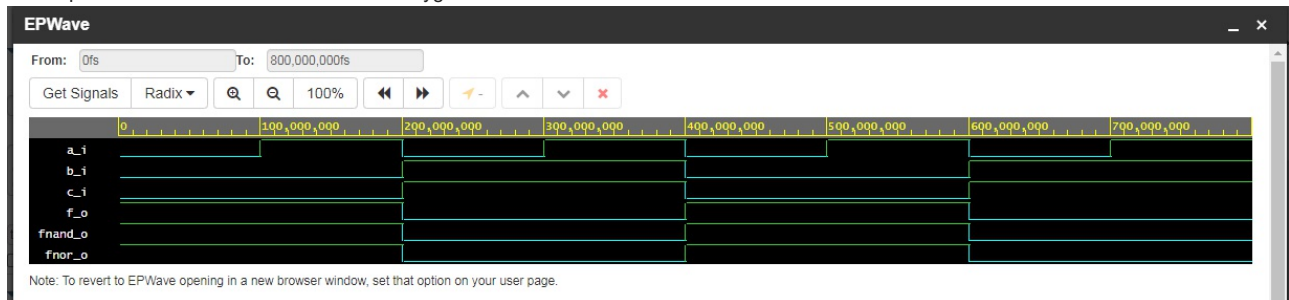And a photo of simulation results in EDA Playground:



We successfully verified De Morgan's laws with function $f(c,b,a)$.

3 Verification of Distributive laws

Parts:

- Listing of VHDL code `design.vhd`,
- Screenshot with simulated time waveforms,
- Link to your public EDA Playground example.

Distributive laws

$$x \cdot y + x \cdot z = x \cdot (y + z)$$


$$(x + y) \cdot (x + z) = x + (y \cdot z)$$

Code from [EDU Playground \(https://www.edaplayground.com/x/8Nx3\)](https://www.edaplayground.com/x/8Nx3)

Excerpt from `design.vhd`:

```
architecture dataflow of gates is
begin
    d1_o <= (x_i and y_i) or (x_i and z_i);
    d2_o <= x_i and (y_i or z_i);
    d3_o <= (x_i or y_i) and (x_i or z_i);
    d4_o <= x_i or (y_i and z_i);
end architecture dataflow;
```

Photo of the simulation results in EDA Playground:

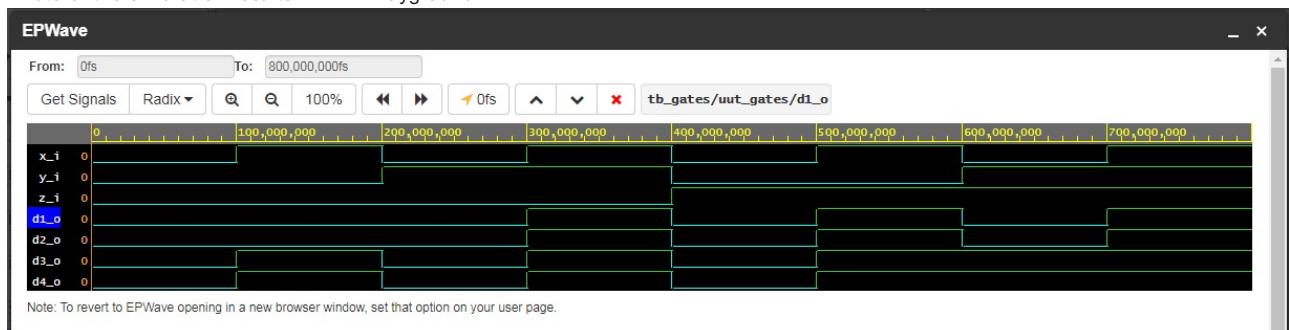

From the simulation it is apparent that $d1$ and $d2$ are equal as well as $d3$ and $d4$ which verifies distributive laws.